

Karnaugh-map Using Arduino

M.DINESH

maddudinesh12@gmail.com

IITH - FUTURE WIRELESS COMMUNICATIONS-(FWC22044)

Contents

Abstract

The objective of this manual is to show how to verify following min-terms. $F = (m_7 + m_2 + m_6 + m_5)$ using karnaugh-map

1 Introduction

Karnaugh-map provides a systematic method for simplifying boolean expressions and may produce simplest SOP or POS expressions.

karnaugh-map used to minimize number of logic gates that are required in a digital circuit.

2 components

component	value	quantity
Arduino	UNO	1
Breadboard	-	1
Led	-	1
Resistor	220ohm	1
Jumperwires	M-M	10

Table-0

3 karnaugh-map

3.1 Implementation

		CD			
		00	01	11	10
AB	00	0	0	0	1
	01	0	1	1	1
	11	0	0	0	0
	10	0	0	0	0

Figure 1:k-map

From the above karnaugh-map the expression is

$$A'BD + A'BC + CD'A'$$

This karnaugh-map is verified by using

Truthtable Table-1

4 Truthtable

A	B	C	D	O/P
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Table-1

5 Hardware Connections

1.connect the arduino to the computer

arduino	2	3	4	5	9	gnd
input	A	B	C	D		
led					+	-

2.The led will ON and OFF when changing the inputs

Table-2

6 Software

Make the connections and connect the Vaman Board to the PC via USB.In the location of choice,type the below commands

1. `svncohttps : //github.com/maddudinesh/iithyderabad-fwc/blob/main/arm_examples/arm_assignment`
2. `cd flash/GCCproject/`
3. `make`

4. `cd ../../`
5. `bash scpsend.shflash`