

Karnaugh-map Using Arduino

M.DINESH

maddudinesh12@gmail.com

IITH - FUTURE WIRELESS COMMUNICATIONS-(FWC22044)

Contents

1	Introduction
2	components
3	karnaugh-map
3.1	Implementation
4	Truthtable
5	Hardware Connections
6	Software

Abstract

The objective of this manual is to show how to verify following min-terms. $F = (m_7 + m_2 + m_6 + m_5)$ using karnaugh-map

1 Introduction

Karnaugh-map provides a systematic method for simplifying boolean expressions and may produce simplest SOP or POS expressions.

karnaugh-map used to minimize number of logic gates that are required in a digital circuit.

2 components

component	value	quantity
Arduino	UNO	1
Breadboard	-	1
Led	-	1
Resistor	220ohm	1
Jumperwires	M-M	10

Table-0

3 karnaugh-map

3.1 Implementation

		CD			
		00	01	11	10
AB	00	0	0	0	1
	01	0	1	1	1
	11	0	0	0	0
	10	0	0	0	0

Figure 1:k-map

From the above karnaugh-map the expression is $A'BD + A'BC + CD'A'$

This karnaugh-map is verified by using

Truthtable Table-1

4 Truthtable

	A	B	C	D	O/P
	0	0	0	0	0
	0	0	0	1	0
	0	0	1	0	1
	0	0	1	1	0
	0	1	0	0	0
	0	1	0	1	1
	0	1	1	0	1
	0	1	1	1	1
	1	0	0	0	0
	1	0	0	1	0
	1	0	1	0	0
	1	0	1	1	0
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	0
	1	1	1	1	0

Table-1

5 Hardware Connections

1.connect the arduino to the computer

arduino	2	3	4	5	9	gnd
input	A	B	C	D		
led					+	-

2.The led will ON and OFF when changing the inputs

Table-2

6 Software

Download the follwing code

<https://github.com/maddudinesh/iithyderabad-fwc/blob/main/assign1-ide/codes/src/main.cpp>