

Karnaugh-map Using Arduino

M.DINESH

maddudinesh12@gmail.com

IITH - FUTURE WIRELESS COMMUNICATIONS-(FWC22044)

Contents

| | |
|-----|--------------------------|
| 1 | Introduction |
| 2 | components |
| 3 | karnaugh-map |
| 3.1 | Implementation |
| 4 | Truthtable |
| 5 | Hardware Connections |
| 6 | Software |

Abstract

The objective of this manual is to show how to verify following min-terms. $F = (m_7 + m_2 + m_6 + m_5)$ using karnaugh-map

1 Introduction

Karnaugh-map provides a systematic method for simplifying boolean expressions and may produce simplest SOP or POS expressions.

karnaugh-map used to minimize number of logic gates that are required in a digital circuit.

2 components

| component | value | quantity |
|-------------|--------|----------|
| Arduino | UNO | 1 |
| Breadboard | - | 1 |
| Led | - | 1 |
| Resistor | 220ohm | 1 |
| Jumperwires | M-M | 20 |

Table-0

3 karnaugh-map

3.1 Implementation

| | | | | | |
|-----------|----|-----------|----|----|----|
| | | <i>CD</i> | | | |
| | | 00 | 01 | 11 | 10 |
| <i>AB</i> | 00 | 0 | 0 | 0 | 1 |
| | 01 | 0 | 1 | 1 | 1 |
| | 11 | 0 | 0 | 0 | 0 |
| | 10 | 0 | 0 | 0 | 0 |

Figure 1:k-map

From the above karnaugh-map the expression is

$$A'BD + A'BC + CD'A'$$

This karnaugh-map is verified by using

Truthtable Table-1

4 Truthtable

| | A | B | C | D | O/P |
|--|---|---|---|---|-----|
| | 0 | 0 | 0 | 0 | 0 |
| | 0 | 0 | 0 | 1 | 0 |
| | 0 | 0 | 1 | 0 | 1 |
| | 0 | 0 | 1 | 1 | 0 |
| | 0 | 1 | 0 | 0 | 0 |
| | 0 | 1 | 0 | 1 | 1 |
| | 0 | 1 | 1 | 0 | 1 |
| | 0 | 1 | 1 | 1 | 1 |
| | 1 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 0 | 1 | 0 |
| | 1 | 0 | 1 | 0 | 0 |
| | 1 | 0 | 1 | 1 | 0 |
| | 1 | 1 | 0 | 0 | 0 |
| | 1 | 1 | 0 | 1 | 0 |
| | 1 | 1 | 1 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 |

Table-1

5 Hardware Connections

| | | | | | | |
|---------|---|---|---|---|---|-----|
| arduino | 2 | 3 | 4 | 5 | 9 | gnd |
| input | A | B | C | D | | |
| led | | | | | + | - |

Table-2

6 Software

- 1.connect the arduino to the computer
- 2.Download the follwing code

<https://github.com/maddudinesh/iithyderabad-fwc/blob/main/fwcassignment1/codes/fwc%20assignment1.txt>

- 3.The led beside the 13th pin ON and OFF when changing the inputs